



Higher National Diploma in Engineering (Electrical and Electronic)

First Year, First Semester Examination – 2017

EE1107- ELECTRICAL PRINCIPLES - A

Instructions for Candidates:

Answer any FIVE (5) questions.

All question carry equal marks.

No. of questions : 06

No. of pages : 04

Time : Three (03) hours

Q1.

- i. The short circuit current through the resistance R_2 is 6A. While network is functioning as normal the current passing through the resistance R_2 is 4A. Calculate the value of E_1 and R_2 of the network given in figure 1. (8 Marks)

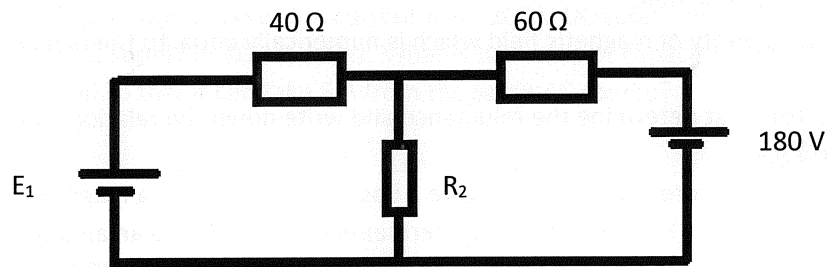


Figure 1

- ii. By using superposition theorem and Kirchoff's laws, find the current through 40 Ω resistor and R_2 of the network given in figure 1. (8 Marks)
- iii. Three 1.5 V, 0.5 A bulbs are connected in parallel. A resistor R is connected in series with the parallel bulb arrangement. This series resistance with 3 parallel bulbs are connected across a 12 V battery having zero internal resistance. Find the value of R in order to light the bulbs with their normal light intensity. (4 Marks)

[Total 20 marks]


Q2.

- i. Write the names of 3 types of capacitors. (3 Marks)
- ii. Draw the graph for the voltage across the capacitance during charging and roughly mark the time constant on the curve. (4 Marks)
- iii. Three capacitors of capacitance $8 \mu\text{F}$, $8 \mu\text{F}$ and $4 \mu\text{F}$ are connected in series and a 12 V volt is applied between the two ends of this combination. Calculate,
 - a. The charges in the $4 \mu\text{F}$ Capacitor. (3 Marks)
 - b. The total energy stored in the combination. (3 Marks)
- iv. Two dielectrics having relative permittivity of k_1 and k_2 , and their thicknesses are t_1 and t_2 . A parallel plate capacitor is completely filled by these two dielectrics. Charge on the plates of the capacitor is Q and the permittivity of air is ϵ_0 . Find the potential difference between two parallel plates. (7 Marks)

[Total 20 marks]

Q3.

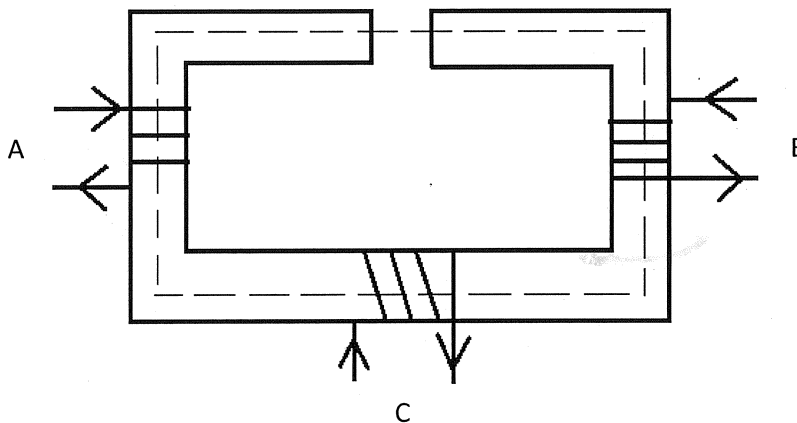- i. State the purpose of magnetic shielding and how the permeability should be of selected material for the shielding. (3 Marks)
- ii. What is the quantity of magnetic field which is numerically equal to the magnetic potential gradient? (1 Marks)
- iii. State 3 factors that determine the reluctance and write down the relationship between them and reluctance. (3 Marks)
- iv. A rectangular iron core shown in the figure 2 has a mean length of a magnetic path of 100 cm, cross section of 2 cm X 2 cm and relative permeability of 1000 and an air gap of 5 mm cut in the core. The three coils carried by the core having number of turns $N_A = 300$, $N_B = 500$ and $N_C = 600$ and the respective currents flowing through the coils are 2 A, 4 A and 3 A. The directions of currents flowing in the coils are shown in the figure. Neglecting the fringing of flux, find,
 - a. Total m.m.f in the circuit
 - b. Total reluctance in the circuit
 - c. Total flux in the circuit
 - d. Flux density in the air gap. (8 Marks)



- v. An iron toroid of 10 cm in diameter and 8 cm^2 in cross section is wound with 300 turns. An exciting current of 2 A is necessary to produce a flux density of 1.2 Wb/m^2 . Calculate the energy stored in the magnetic field. (5 Marks)

[Total 20 marks]

Q4

- i. Why does the average power absorbed by a R-L- C circuit is equal to I^2R ? (2 Marks)
- ii. What do you mean by lagging power factor? (1 Mark)
- iii. If the supply frequency is increased, state with reasons whether the reactance of a circuit is increased or decreased when the circuit consists of,
- a. Choking coil
 - b. Capacitor
- (4 Marks)
- iv. Derive an equation for the resonant frequency f_c of a R-L-C series circuit, having an inductance L, capacitance C, and Resistance R (3 Marks)
- v. Write a relationship between the peak value and the rms value of an alternating sinusoidal current or voltage. (2 Mark)
- vi. The coil of an electromagnet takes 5 A current from 200 V DC supply but it takes only 2.5 A current from an AC supply of 200 V, 50 Hz. What is the value of capacitor to be connected in series with the coil so that it can take 5 A from the same AC source? (8 Marks)

[Total 20 marks]

Q5.

Two impedances are given by $Z_1 = (10 \Omega - j5 \Omega)$ and $Z_2 = (8 \Omega + j6\Omega)$ are connected in parallel and connected across a voltage of 200 V.

- i. What is the total current taken by the circuit (4 Marks)
- ii. What is the current taken by each branch (4 Marks)
- iii. Find the average power delivered to the circuit (3 Marks)
- iv. What is the power taken by each branch ? (3 Marks)
- v. Calculate the power factor of individual circuit and of combination. (3 Marks)
- vi. Draw the vector diagram (3 Marks)

[Total 20 marks]

Q6.

- i. Re-draw the diagram shown in figure 3 and mark the voltages and currents without changing its properties. (2 Marks)

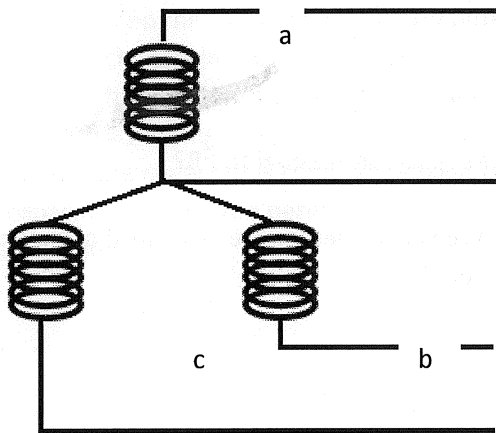


Figure 3

- ii. Draw the complete phasor diagram of three phase star connection to indicate the phase voltages and line voltages. Use the double subscript notation. (3 marks)
- iii. Why is the delta system is more suitable to transmit electrical power than a star system (2 Marks)
- v. Non inductive non capacitive balanced delta connected to 3 phase load consumes 12 kW power. The phase current drawn by the load is 10 A. Find the line voltage and magnitude of load in a phase. (5 Marks)
- vi. Three similar single phase circuits each consisting of a fluorescent lamp of 0.04 H of negligible resistance are connected in star to a 3 phase, 50 Hz AC supply 400 V between lines. Calculate the line current. If they are now connected in delta, calculate the line current and the current taken by each lamp. Prove that the power absorbed by 3 phases when connected in mesh is 3 times the power absorbed by 3 phases when connected in star through this Answer. [Hint : Fluorescent lamp is purely resistive, each phase consist of a resistance and an inductance in series.] (8 Marks)

[Total 20 marks]

Q6.

- i. Re-draw the diagram shown in figure 3 and mark the voltages and currents without changing its properties. (2 Marks)

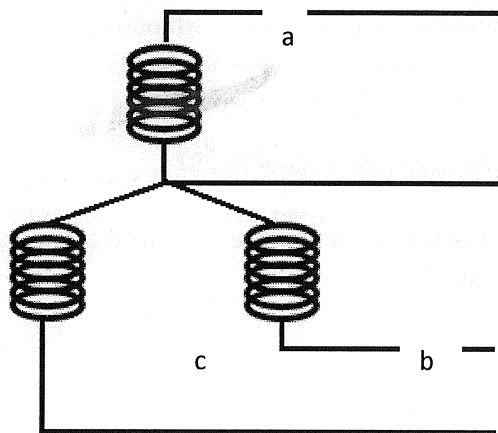


Figure 3

- ii. Draw the complete phasor diagram of three phase star connection to indicate the phase voltages and line voltages. Use the double subscript notation. (3 marks)
- iii. Why is the delta system is more suitable to transmit electrical power than a star system (2 Marks)
- v. Non inductive non capacitive balanced delta connected to 3 phase load consumes 12 kW power. The phase current drawn by the load is 10 A. Find the line voltage and magnitude of load in a phase. (5 Marks)
- vi. Three similar single phase circuits each consisting of a fluorescent lamp of 0.04 H of negligible resistance are connected in star to a 3 phase, 50 Hz AC supply 400 V between lines. Calculate the line current. If they are now connected in delta, calculate the line current and the current taken by each lamp. Prove that the power absorbed by 3 phases when connected in mesh is 3 times the power absorbed by 3 phases when connected in star through this Answer. [Hint : Fluorescent lamp is purely resistive, each phase consist of a resistance and an inductance in series.] (8 Marks)

[Total 20 marks]